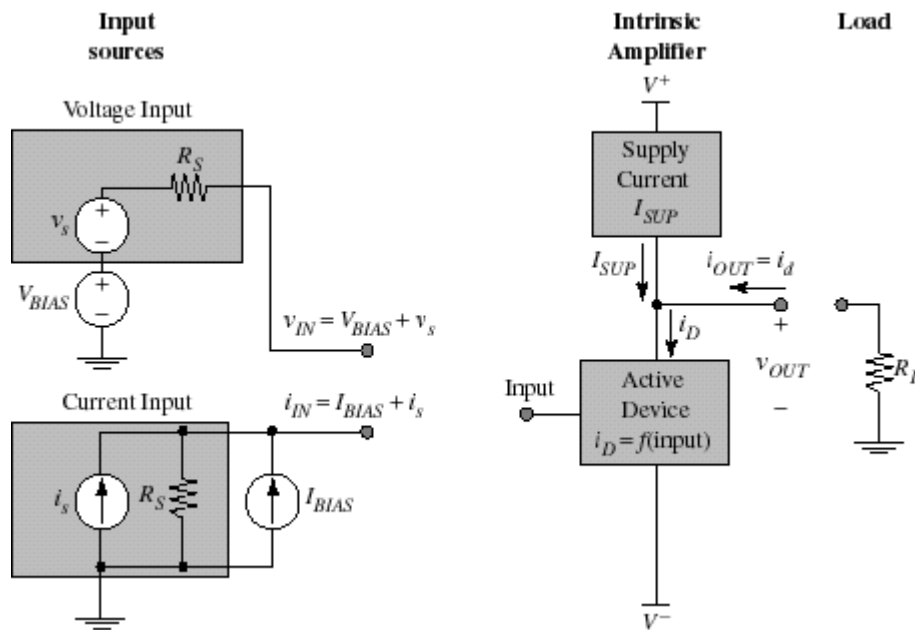


# Generalized Transistor Amplifier

- \* Perspective: look at the various configurations of bipolar and MOS transistors, for which a *small-signal* voltage or current is transformed (e.g., usually *amplified* -- increased in magnitude) between the input and output ports.
- \* Amplifier terminology:



## Abstractions:

*Sources* include precisely adjusted bias voltages or currents

Source resistance is associated with the small-signal source

*Load resistance* typically models another amplifier, speaker, actuator, etc.

## Amplifier Biasing

- \* Input bias voltage  $V_{IN}$  sets the DC device current,  $I_D$  to precisely equal the supply current  $I_{SUP}$   
(note --  $D = \text{“device”}$  here)
- \* Likewise, if the input is the sum of small-signal and DC current sources, then the input bias current  $I_{BIAS}$  is chosen so that it sets  $I_D = I_{SUP}$   
The DC output current is  $I_{OUT} = I_D - I_{SUP} = 0$  A,  
which implies that the DC output voltage  $V_{OUT} = 0$  V also.

Note: both positive and negative DC supply voltages are used so  $V_{OUT} = 0$  V does *not* mean that the DC voltage drop is zero!

**KEY IDEA:** the small-signal voltage or current source perturbs the amplifier bias, through  $i_D = f(\text{input})$ , which results in a small-signal output current

$$i_{OUT} = i_D - i_{SUP} = (I_D + i_d) - I_{SUP} = i_d$$

since the supply current is DC ( $i_{SUP} = I_{SUP}$ )


A small-signal output voltage is generated

$$v_{out} = -R_L i_{out}, \text{ where } R_L \text{ is the load resistor}$$


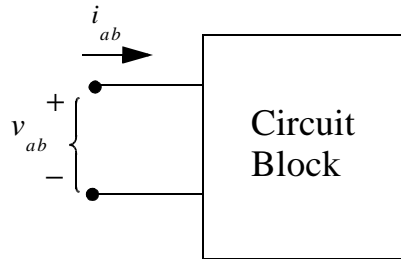
# Source and Load Models are “One-Ports”

- \* What is a “port”?

a terminal pair  
across which a  
voltage and associated  
current are defined



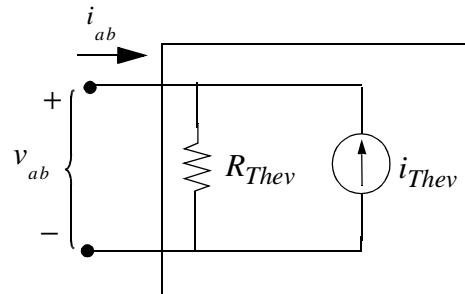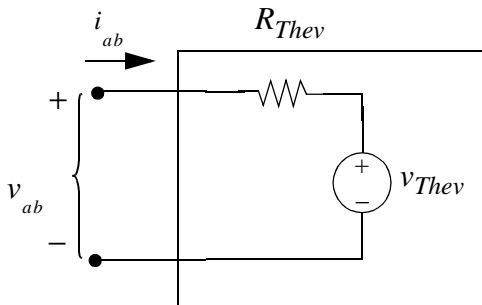
- \* If the circuit block contains only linear elements, then it can be represented as (according to Thevenin's and Norton's Theorems)



We have “one-port” models for the source and load ...

what about for the amplifier block?
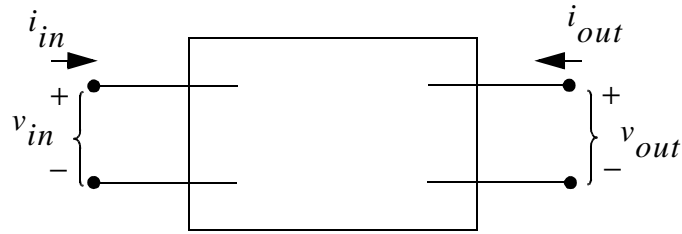
## Small-Signal *Two-Port* Models for Amplifier Blocks



Linear and Unilateral } If  $v_{in} = 0, i_{in} = 0$   
 and } and  
 }  $i_{in} \propto v_{in}$

$$\frac{v_{in}}{i_{in}} \equiv R_{in}$$

But, output depends linearly on what's connected both at input and output: ( $\alpha$ s are constants)

$$\left. \begin{array}{l} \text{e.g., } i_{out} = \alpha_1 v_{in} + \alpha_2 v_{out} \quad (1) \\ \text{or } i_{out} = \alpha_3 i_{in} + \alpha_4 v_{out} \quad (2) \\ \text{or } v_{out} = \alpha_5 v_{in} + \alpha_6 i_{out} \quad (3) \\ \text{or } v_{out} = \alpha_7 i_{in} + \alpha_8 i_{out} \quad (4) \end{array} \right\} \begin{array}{l} \text{ALL EQUIVALENT} \\ \text{(only need one)} \end{array}$$

## Two-Port Amplifier Models

- \* How do we characterize an amplifier's response to a general input signal (Thévenin or Norton source)?

the controlled source is determined by output signal  
(voltage or current ... we select which is of interest) and by the input signal

Therefore, there are **FOUR** types of amplifiers:

Voltage

Current

Transconductance (voltage in, current out)

Transresistance (current in, voltage out)

- \* We need *methods* to find the parameters for these four models for a particular transistor amplifier configuration:


$R_{in}$  = Input Resistance       $R_{out}$  = Output Resistance

$A_v$  = Voltage Gain       $A_i$  = Current Gain


$G_m$  = Transconductance       $R_m$  = Transresistance

# Two-Port Small-Signal Amplifiers


Voltage Amplifier

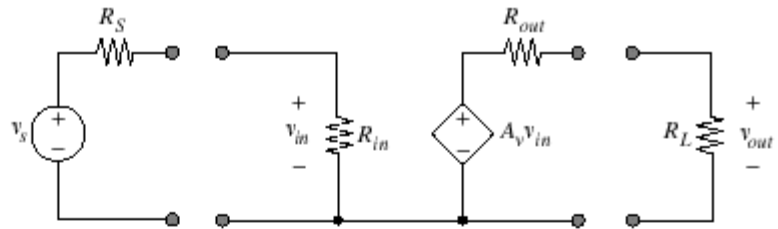


Current Amplifier

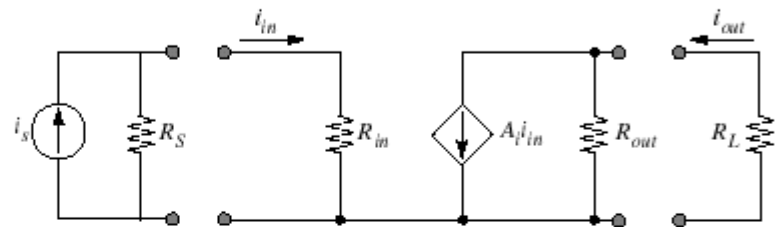

Transconductance Amplifier

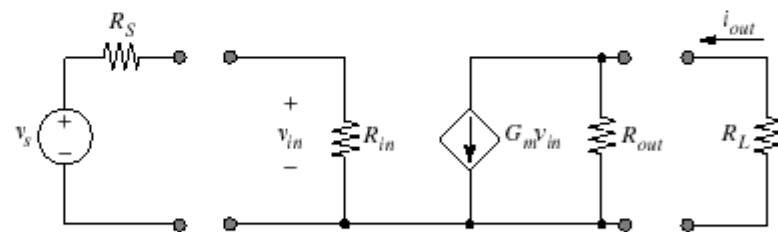


Transresistance Amplifier

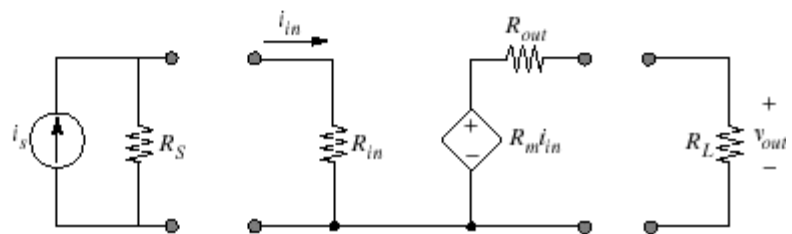

## Input Resistance $R_{in}$


- \* Define systematic procedures to find the two-port parameters
- \* **Key idea:** leave the *load* resistance  $R_L$  attached when finding  $R_{in}$
- \* Apply a small-signal *test source* (voltage source **or** current source) and compute (using KVL, KCL, or inspection) the resulting current or voltage:

$$R_{in} = \frac{v_t}{i_t}$$

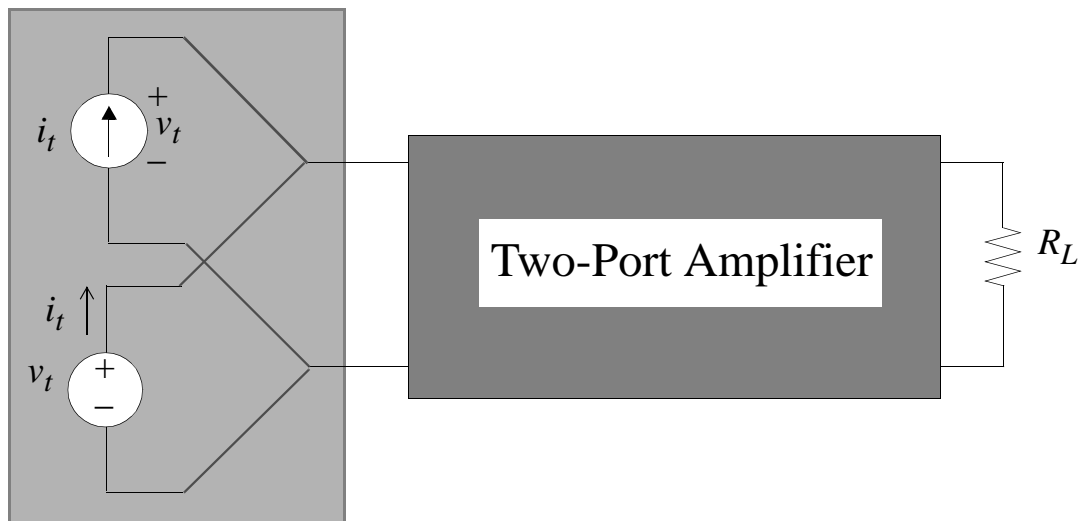
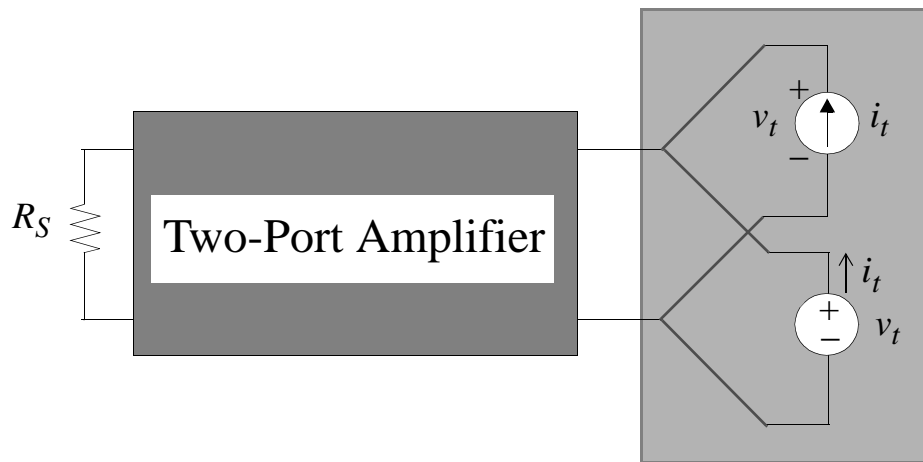
## Output Resistance $R_{out}$


- \* Remove  $R_L$ ; leave the source resistance attached when finding  $R_{out}$




$$R_{out} = \frac{v_t}{i_t}$$
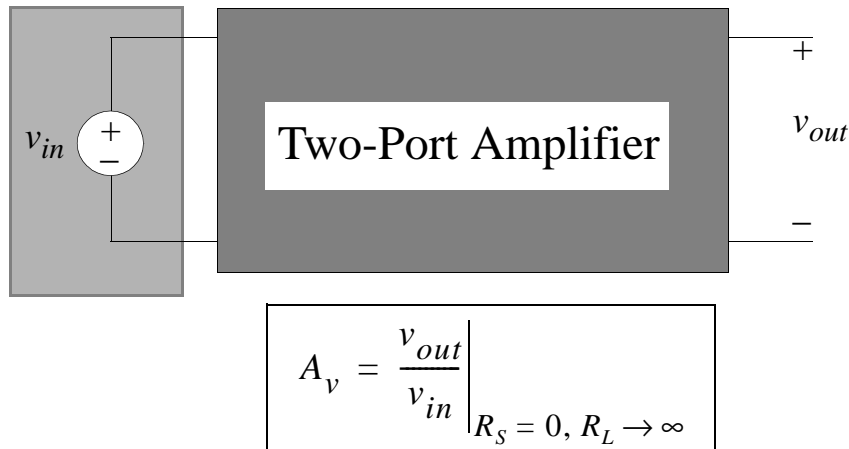
## Voltage Gain $A_v$ and Current Gain $A_i$

- \* **Voltage gain:** open-circuit the output port ( $R_L \rightarrow \infty$ ) and short the source resistance ( $R_S \rightarrow 0 \Omega$ ) to find the unloaded voltage gain  $A_v$ :




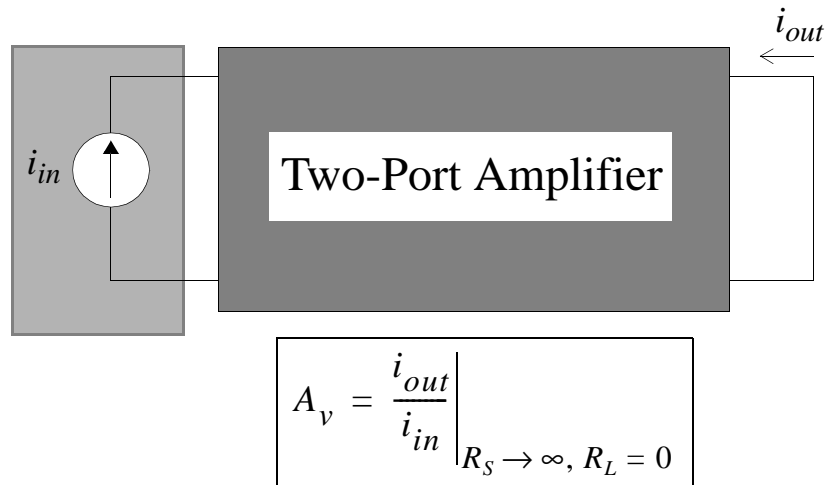- \* **Current gain:** short-circuit the output port ( $R_L \rightarrow 0 \Omega$ ) and open-circuit the source resistance ( $R_S \rightarrow \infty$ ) to find the short-circuit current gain  $A_i$ :



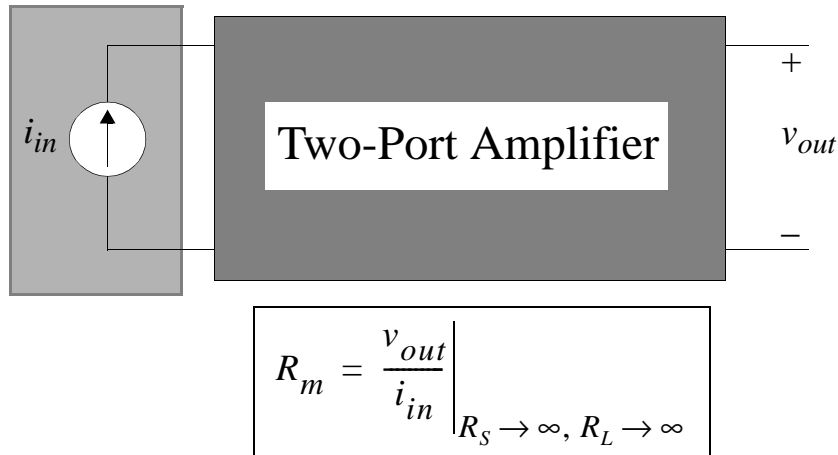
## Transresistance $R_m$ and Transconductance $G_m$

- \* Open-circuit the source resistance ( $R_S \rightarrow \infty$ ) and open-circuit the output port ( $R_L \rightarrow \infty$ ) to find the transresistance  $R_m$ :



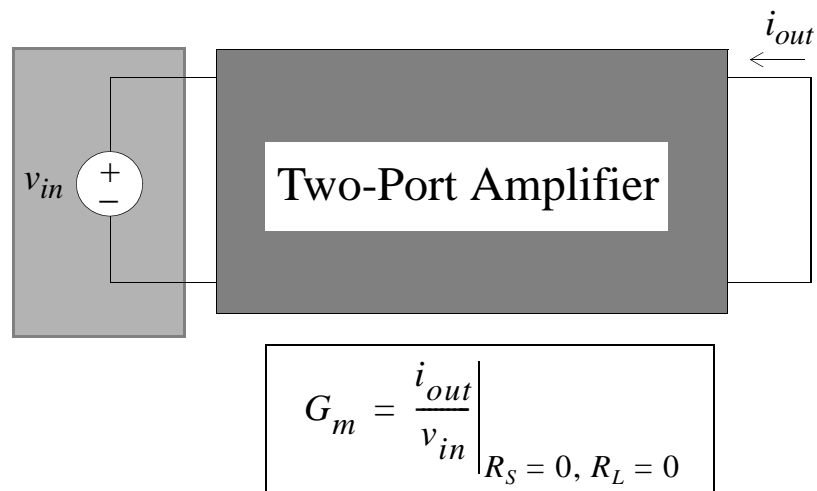- \* Short-circuit the input resistance ( $R_S = 0 \Omega$ ) and short-circuit the output port ( $R_L = 0 \Omega$ ) to find the transconductance  $G_m$ :



- \* Note that the source resistor  $R_S$  and the load resistor  $R_L$  are *disconnected* for determining the bias point