

CS 121: Lecture 4

Defining Computation: Circuits

Madhu Sudan


<https://madhu.seas.harvard.edu/courses/Fall2020>

Book: <https://introtcs.org>

How to contact us { The whole staff (faster response): [CS 121 Piazza](#)
Only the course heads (slower): cs121.fall2020.course.heads@gmail.com


Reminder

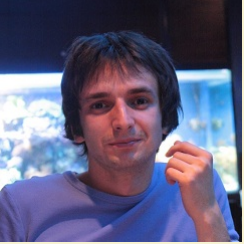- Homework 1 due Thursday!
- CS 121.5: [Sasha Golovnev](#) on “circuit lower bounds” on Thursday.
- Reminder: Sign up for active participation, Lectures 8-11.
- Other modes of participation: Sections+OH+Piazza!
 - TFs standing by!!




What


$a, b \in \mathbb{N}$

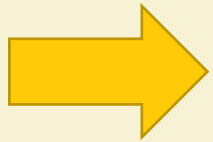

input

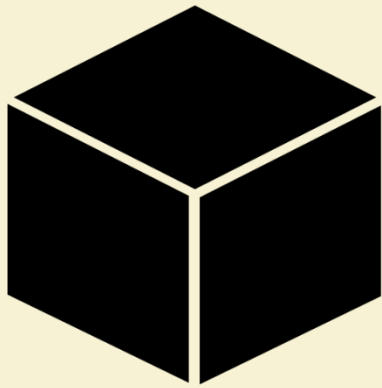

$a \cdot b$

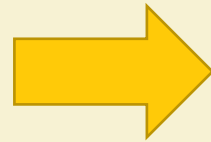

output

Function

How

Input: $a, b \in \mathbb{N}$

Operations:

$res \leftarrow 0$

for $i = 1 \dots \#digits(a)$:

for $j = 1 \dots \#digits(b)$:

$res \leftarrow res + 10^{i+j} a_i b_j$

return res

Formula/Algorithm/
Program/Circuit/..

How

Input: $a, b \in \mathbb{N}$

Operations:

$res \leftarrow 0$

for $i = 1 \dots \#digits(a)$:

for $j = 1 \dots \#digits(b)$:

$res \leftarrow res + 10^{i+j} a_i b_j$

return res

Formula/Algorithm/
Program/Circuit/.

Example:

$f: \{0,1\}^n \rightarrow \{0,1\}^m$ finite function

x	$f(x)$
000	0
001	1
010	1
011	0
100	1
101	0
110	0
111	1

Compute f :

map x to $f(x)$ using sequence of "basic operations".

Today's goals


- Define "basic operations".
- Formally define " f can be computed using the basic operations"
- Formally define " f can be computed using $\leq s$ operations"

Basic Operations

$AND, OR : \{0,1\}^2 \rightarrow \{0,1\}, NOT : \{0,1\} \rightarrow \{0,1\}$


$$AND(a, b) = a \wedge b = \begin{cases} 1, & a = b = 1 \\ 0, & \text{otherwise} \end{cases}$$

a, b	$a \wedge b$
00	0
01	0
10	0
11	1

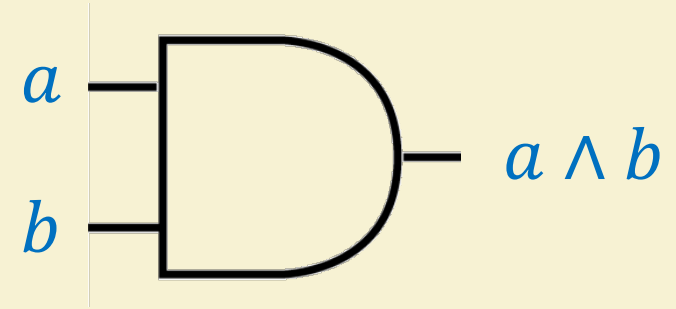


$$OR(a, b) = a \vee b = \begin{cases} 0, & a = b = 0 \\ 1, & \text{otherwise} \end{cases}$$

a, b	$a \vee b$
00	0
01	1
10	1
11	1

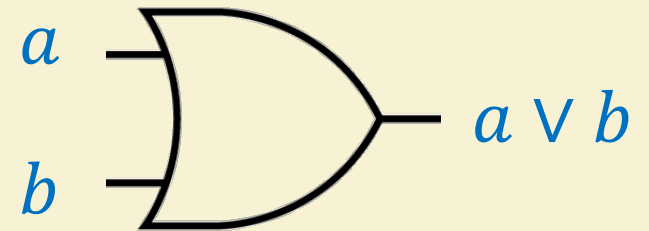

$$NOT(a) = \neg a = \bar{a} = \begin{cases} 1, & a = 0 \\ 0, & a = 1 \end{cases}$$

a	$\neg a$
0	1
1	0

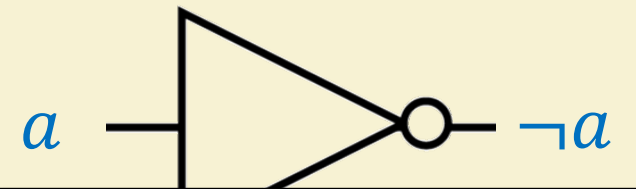

Continue on Jupyter

Circuit = Sequence of Basic Operations

- Two equivalent ways of thinking:
 - As a graph
 - As a “straightline” program (no loops – simple sequence of instructions).

(AON)-Circuit Computing Majority

Circuit = Sequence of Basic Operations

Two equivalent ways of thinking:

As a graph

As a "straightline" program (no loops – simple sequence of instructions).


Exercise Break 1

- Describe circuit computing Exactly-2: $\{0,1\}^3 \rightarrow \{0,1\}$:
 - Exactly-2(x_0, x_1, x_2) = 1 \Leftrightarrow $x_0 + x_1 + x_2 = 2$
 - How many gates did you use?
- Food for thought/If you have extra time:
 - How would you extend to circuit computing Exactly- m : $\{0,1\}^n \rightarrow \{0,1\}$ given by Exactly- m ($x_0 \dots x_{n-1}$) = 1 \Leftrightarrow $x_0 + \dots + x_{n-1} = m$.
 - How many gates would Exactly- m require? (say if $m \cong \frac{n}{2}$)

NAND Operation

$$\text{NAND}(a, b) = \overline{a \wedge b} = \begin{cases} 0, & a = b = 1 \\ 1, & \text{otherwise} \end{cases}$$

a, b	$\overline{a \wedge b}$
00	1
01	1
10	1
11	0

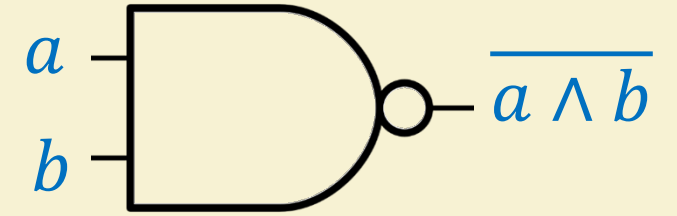


Exercise (Part 1): Show how to compute *NAND* using *AND*, *OR*, *NOT*

Corollary: If we can compute f using combinations of *NAND* then we can compute f using *AND/OR/NOT*

NAND Operation

$$\text{NAND}(a, b) = \overline{a \wedge b} = \begin{cases} 0, & a = b = 1 \\ 1, & \text{otherwise} \end{cases}$$


a, b	$\overline{a \wedge b}$
00	1
01	1
10	1
11	0

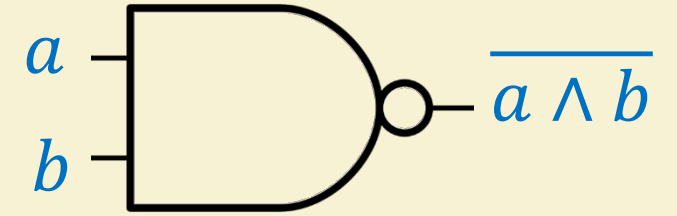


Exercise (Part 2): Show how to compute (1) *NOT*, (2) *AND*, (3) *OR* using *NAND*

Corollary: If we can compute f using combinations of *AND/OR/NOT* then we can compute f using *NAND*

f computable by
 $\leq s$ *NANDs*

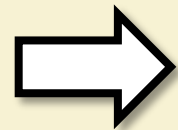

f computable by
 $\leq 2s$ *AND/OR/NOT*

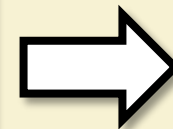

f computable by
 $\leq 6s$ *NANDs*

Exercise Break 2:

Exercise 1: Compute NOT, AND, OR using NAND
(how many gates per operation?)


Exercise 2: Compute NAND using AND, OR, NOT
(how many gates per operation?)

Food for thought:

- Did you use all three gates in Exercise 2? If not what do you learn from this?

Boolean Circuits

(with \wedge, \vee, \neg gates)

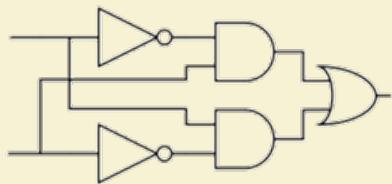


AON-CIRC

straightline programs


(with AND, OR, NOT operations)
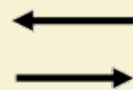
```
t1 = AND(X[0], X[1])
notx0 = NOT(X[0])
t2 = AND(notx0, X[2])
Y[0] = OR(t1, t2)
```



NAND Circuits

(with $\bar{\wedge}$ gates)

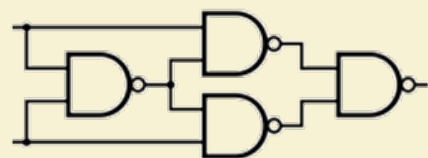


NAND-CIRC

straightline programs

(with NAND operation)
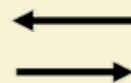
```
u = NAND(X[0], X[1])
v = NAND(X[0], u)
w = NAND(X[1], u)
Y[0] = NAND(v, w)
```



...

Universality-1

- Have seen $\{AND, OR, NOT\} \equiv \{NAND\}$
 - $f: \{0,1\}^n \rightarrow \{0,1\}^m$ has $\{AND, OR, NOT\}$ -circuit iff it has $\{NAND\}$ -circuit
- Is $\{NOT\} \equiv \{NAND\}$?
- Is $\{AND, OR\} \equiv \{NAND\}$?
- Is $\{AND, NOT\} \equiv \{NAND\}$?
- Is $\{AND, XOR\} \equiv \{NAND\}$? Is $\{AND, XOR\} \equiv \{AND, OR, NOT\}$?
 - Not immediate, but same answer!

Universality-2

- Let $S = \{f_1, \dots, f_\ell\}$ be Boolean functions, $f_i: \{0,1\}^{k_i} \rightarrow \{0,1\}$.
- S -circuit is a sequence of operations where each operation is of the form $z = f_i(y_1, \dots, y_{k_i})$ - where y_1, \dots, y_{k_i} input or previously computed.
- S is (NAND-)Universal iff there exists an S -circuit computing $\text{NAND}(x_0, x_1)$.
- Can define $\{AND, OR, NOT\}$ -Universal similarly.
 - $(\exists S$ -circuit computing AND, $\exists S$ -circuit computing OR, $\exists S$ -circuit computing NOT)
 - S is $\{AND, OR, NOT\}$ -Universal iff S is $\{NAND\}$ -Universal.
 - So ... abbreviate to " S is Universal".

Summary:

- “Basic operations”: $\{NAND\}$ (or equivalently $AON = \{AND, OR, NOT\}$).
- “ f can be computed with basic operations”: \exists NAND-circuit computing f
 - Or equivalently NAND-CIRC program, or AON circuit, or AON-CIRC program.
- “ f can be computed with $\leq s$ basic operations”:
 - \exists NAND-circuit program with $\leq s$ gates computing f
 - Or equivalently NAND-CIRC program with $\leq s$ lines
- S is universal iff $\exists S$ -circuit computing NAND.
 - Exercise: S is universal $\Rightarrow \exists c$ such that the following holds for every f
 - if f can be computed with $\leq s$ basic operations, then f can be computed by an S -circuit with at most cs gates.

Next Lecture

- Every function $f: \{0,1\}^n \rightarrow \{0,1\}$ can be computed by basic operations.
- NAND-universality is really universal!!
- Every function f can be computed by circuit with $O(n2^n)$ -gates.
(complexity upper bound)
- Some (most!) functions require $\Omega\left(\frac{2^n}{n^2}\right)$ -gates. (Complexity lower bound.
Limits of circuits!)